


King Saud University College of Computer and Information Sciences Computer Science Department		 جامعة الملك سعود King Saud University College of Computer & Information Sciences Computer Science Department		
Course Code	CSC 220			
Course Title	Computer Organization			
Semester	S1 – 1443 (Fall-2021)			
Exam	Midterm 1			
Date	24/10/2021	Duration	90 minutes	
Student Name				
Student ID				
Section No.				
Course Learning Outcomes		Relevant question	Full mark	Student mark
CLO 1.1	Data Representation	1	8	
CLO 1.2	Digital circuit design and simplification	2	6	
CLO 1.2	Digital circuit design and simplification	3	5	
CLO 2.1	Combinational and sequential circuits design	4	6	
Total			25	
Feedback/Comments:				
<div style="border: 1px solid black; border-radius: 50%; padding: 20px; text-align: center;"> <p>Codingwithus.net</p> <p>00201157933898</p> <p>tel: @Mostafa massoud.</p> </div>				

$E \rightarrow 14 \rightarrow 1110$
 $F \rightarrow 15 \rightarrow 1111$
 $C \rightarrow 12 \rightarrow 1100$

Question 1. (8 Marks)

Q#1.a Marks 4

1) Write octal number corresponds to the hexadecimal number EF.C

(357.6)₈

2) Write Binary number that corresponds to the decimal number 45.125

(101101.001)₂

3) Write BCD code corresponds to the binary number 1101.1

(0001 0011 . 0101)_{BCD}

4) Write The decimal number corresponds to the octal number 21.4

(17.5)₁₀

$(E F . C)_{Hex}$
 $\downarrow \downarrow \leftarrow$
 $(1110)(1111).(1100)_2$
 $\leftarrow (357.6)_8$

السؤال في الخلف

Mostafa(codingwithus.net)

Q#1.b

Write smallest and largest Positive and negative number represented in 6 bits representation in 2's complement. Mark 1

Ans: Largest: +31

$$+(2^{n-1} - 1) = +2^5 - 1 = +31$$

Smallest: -32

$$\rightarrow -2^{n-1} = -2^5 = -32$$

Q#1.C

Complete following Table

Marks 3


A	A in Sign Magnitude (8 bits)	A in 1's Comp. (8 bits)	A in 2's comp. (8 bits)
10	00001010	00001010	00001010
-1	10000001	11111110	11111111
-7	10000111	11111000	11111001

$$+1 = 00000001$$


$$+7 = 00000111$$

Question 2 (6 Marks: 2+2+2)

(a) Suppose A and B are input waveform for a NOR Gate, show the output waveform X

NOR 1
 NOR 2
 A \rightarrow 

A	B	A+B	A+B
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

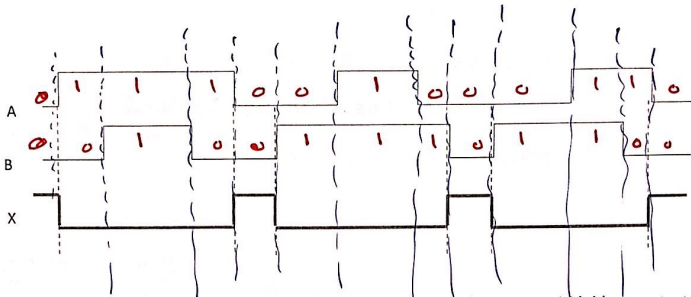

(b) Suppose a combinational circuit accepts a 3-bit binary number and generate a 4-bit binary output equal to double of the input number (e.g. if input is 011 the output is 0110).

- Write the truth table for the function
- Represent the functions in SOP form (without simplification).

Answer of Question 2 (b)

			output			
A	B	C	w	x	y	z
0	0	0	0	0	0	0
1	0	0	0	0	1	0
2	0	1	0	1	0	0
3	0	1	0	1	1	0
4	1	0	1	0	0	0
5	1	0	1	0	1	0
6	1	1	1	1	0	0
7	1	1	1	1	1	0

$$w = \sum m(4, 5, 6, 7)$$

$$x = \sum m(2, 3, 6, 7)$$

$$y = \sum m(1, 3, 5, 7)$$

$$z = 0$$

Codingwithus.net
00201157933898
tel: @Mostafamassoud

Question 3 (5 Marks: 2+1+2)

- (a) Find the Simplified function of Boolean function F together with the don't-care conditions d in sum-of-products form

$$F(w, x, y, z) = \sum (0, 1, 2, 3, 7, 8, 10)$$

$$d(w, x, y, z) = \sum (5, 6, 11, 15)$$


(b) Find the Simplified function of the following Boolean function in sum-of-products form by means of a four-variable k-map.

$$F(w, x, y, z) = \sum m(0, 1, 8, 9, 10, 12, 13)$$

$$f(A, B, C, D) =$$


(c) Draw the logic diagram of simplified function of (b) with NAND gates only.

مبسطه با در

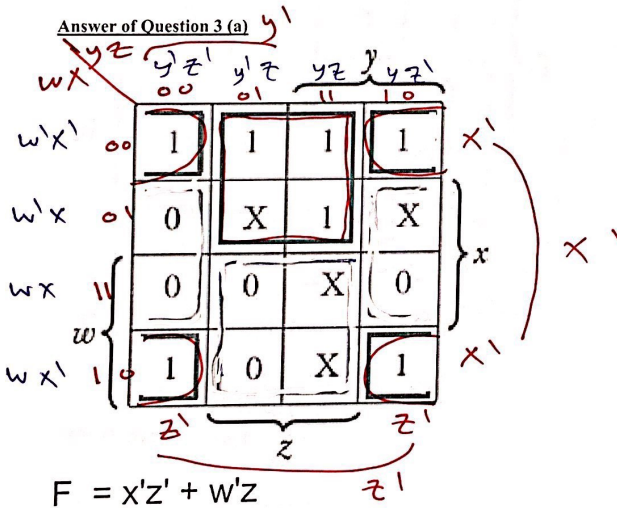


Answer of Question 3 (b)

Mostafa(codingwithus.net)

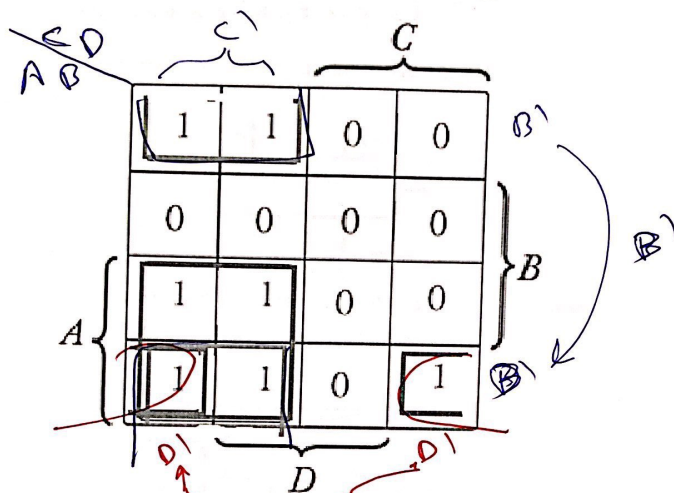


$$F = AC' + B'C' + AB'D'$$

Answer of Question 3 (c)

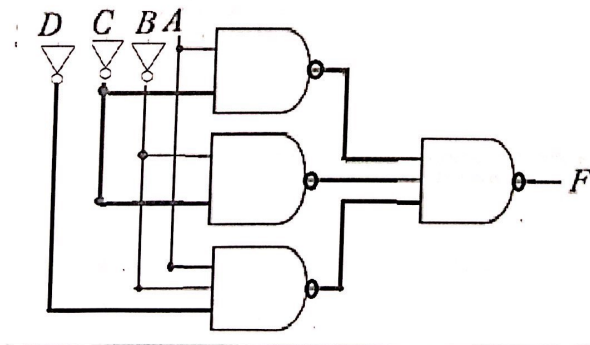

Question 4 (6 Marks: 2+2+2) *ch5*

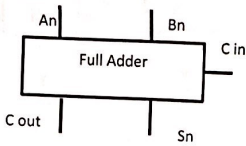(a) Consider the following bloc diagram of a full-addder



Give the truth table of the circuit and drive the output expressions of S_n and C_{out} .

An	Bn	Cin	Sn	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


بعض

$$C_{out} = (A_n \oplus B_n)C_{in} + A_n B_n$$


$$S = A_n \oplus B_n \oplus C_{in}$$

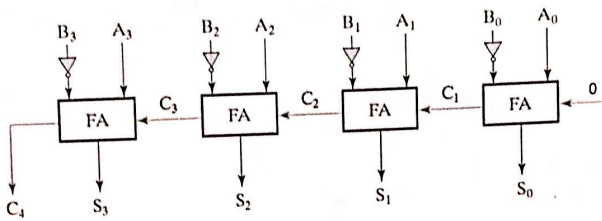(b) Using this circuit show how can we built a circuit capable of performing the subtraction, using 2's complement method, between two words A and B of 4 bits each one.

Codingwithus.net
00201157933898
tel: @Mastafmassoud



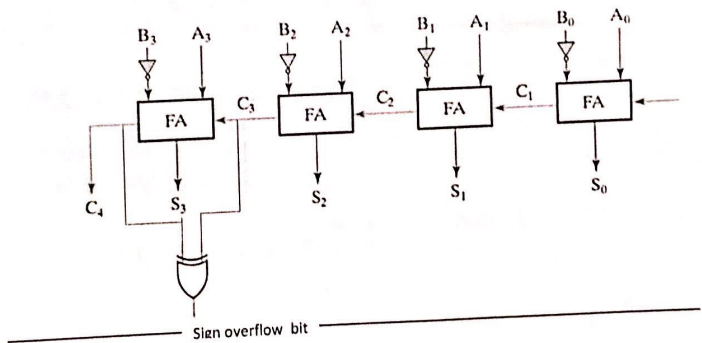(c) Give a solution to detect sign overflow for the circuit that is proposed in (b)



Mostafa(codingwithus.net)

THE END

$$\underline{Q_1 - Q_2 - 2}$$

$$(45.125)_{10} = (\quad ? \quad)_2$$

يوجد لها طريقتان للحل :

الطريقة الأولى بالجداول

32	16	8	4	2	1	0.5000	0.2500	0.1250	
1	0	1	1	0	1	0	0	1	

$$45 - 32 = 13$$

$$13 - 8 = 5$$

$$5 - 4 = 1$$

$$\therefore (45.125)_{10} = (101101.001)_2$$

الطريقة الثانية : بالمسح الجزر الصحيح والجزء الكسري.

$$\begin{array}{r|l}
 2 & 45 \quad 1 \quad \uparrow \\
 2 & 22 \quad 0 \\
 2 & 11 \quad 1 \\
 2 & 5 \quad 1 \\
 2 & 2 \quad 0 \\
 2 & 1 \quad 1 \\
 2 & 0
 \end{array}$$

$$\begin{array}{l}
 \boxed{0.250} = 2 \times 0.125 \\
 \boxed{0.500} = 2 \times 0.250 \\
 \boxed{1.0} = 2 \times 0.500
 \end{array}$$

$$\therefore (45.125)_{10} = (101101.001)_2$$

$$\varphi_1 - a - 3$$

$$(1101.1)_2 = (\quad ? \quad)_{BCD}$$

نقل العشري كوسيط

① تحويل البايزي لعشري

② تحويل العشري ل BCD

تذكر انه لا BCD لا يقبل نظام تحويل له الا العشري

8	4	2	1	.	0.5000
1	1	0	1	.	1

$$8 + 4 + 1 + 0.5 = (13.5)_{10}$$

$$(00010011.0101)_{BCD}$$

$$\varphi_1 - a - 4$$

$$(21.4)_8 = (\quad)_{10}$$

يوجد طريقتين للحل: اول تحويل Binary كوسيط ثم لعشري

$$(21.4)_8 = (01000101.100)_{2}$$

16	8	4	2	1	.	0.5000
1	0	0	0	1	.	1

$$= 16 + 1 + 0.5 = (17.5)_{10}$$

الطريقة الثانية: Mostafa(codingwithus.net)

بالفرد في قوس العدد 8

$$(21.4)_8 = 2 \times 8^1 + 1 \times 8^0 + 4 \times 8^{-1}$$

$$= 16 + 1 + \frac{4}{8} = (17.5)$$